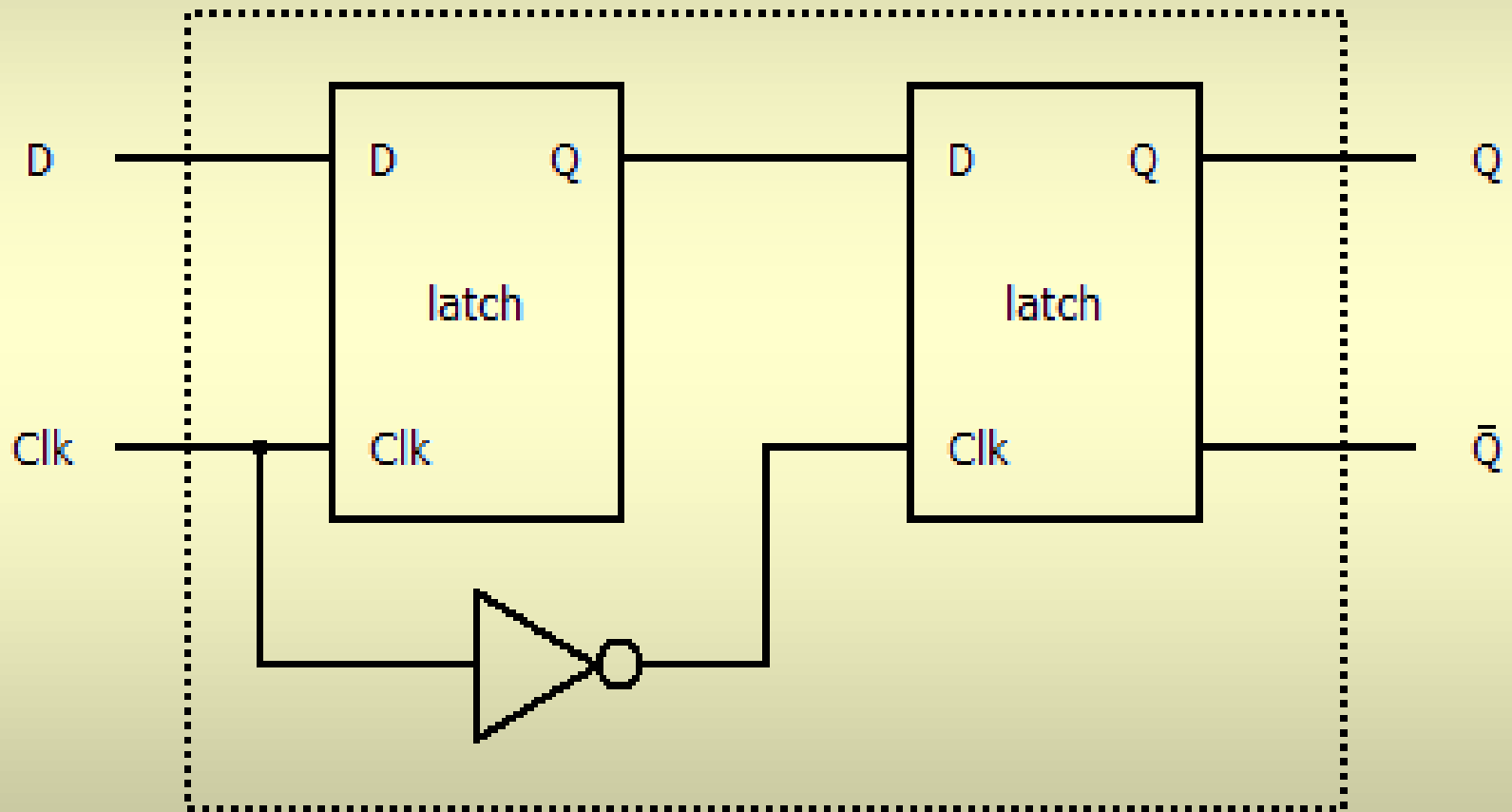


Flip-flop

- inputs are considered on the rising (or falling) edge of the clock signal
- ways of making a flip-flop
 - electronics - derive the clock signal
 - results in an impulse-like signal
 - use latches → master-slave circuits

Master-slave D Flip-flop



Latch vs. Flip-flop

- each category has its utility
- flip-flops - used for controlling digital systems
 - the edge of the clock signal is very short compared with the clock period
 - i.e., it can be considered as a moment
 - during each clock period, the system makes exactly one step of its evolution
- latches - asynchronous systems


III.2. Complex Sequential Circuits

Registers

- a bistable circuit implements a single bit
 - not very useful in practice
- we can use several bistable circuits together
 - all receive the same command at the same time
 - such a circuit is called register
- types of registers
 - parallel registers
 - shift (serial) registers


Parallel Register

 - implementation with D bistable circuits
 - can be latches or flip-flops, as needed
- the same command (clock)
 - all bits change at the same moments
- natural extension of the bistable circuit





Classic Shift Register

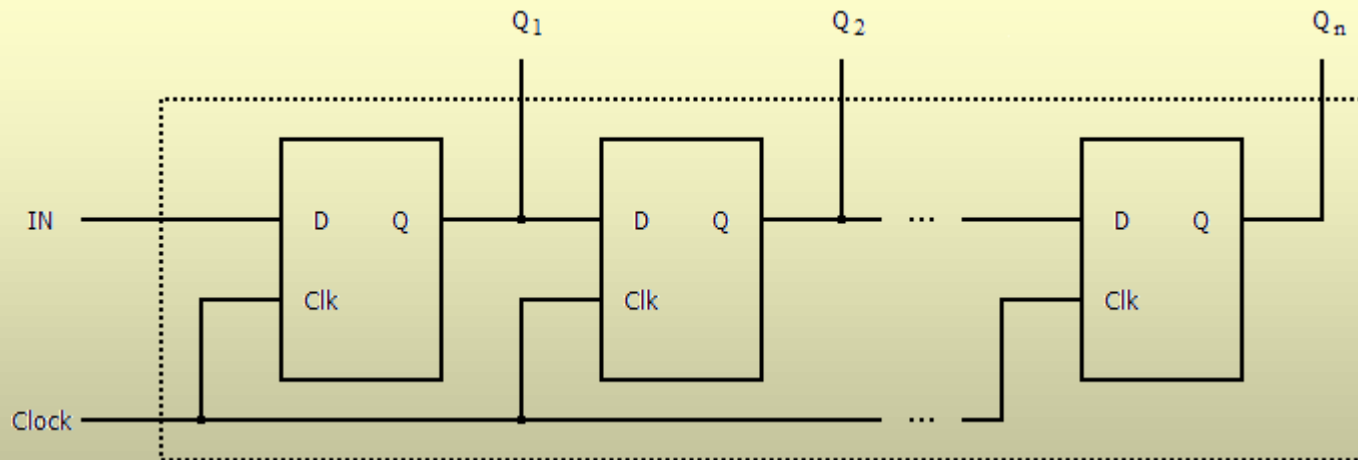- memorizes the last n values applied on the input
- can be implemented only with flip-flops
 - homework: why?




Other Shift Registers

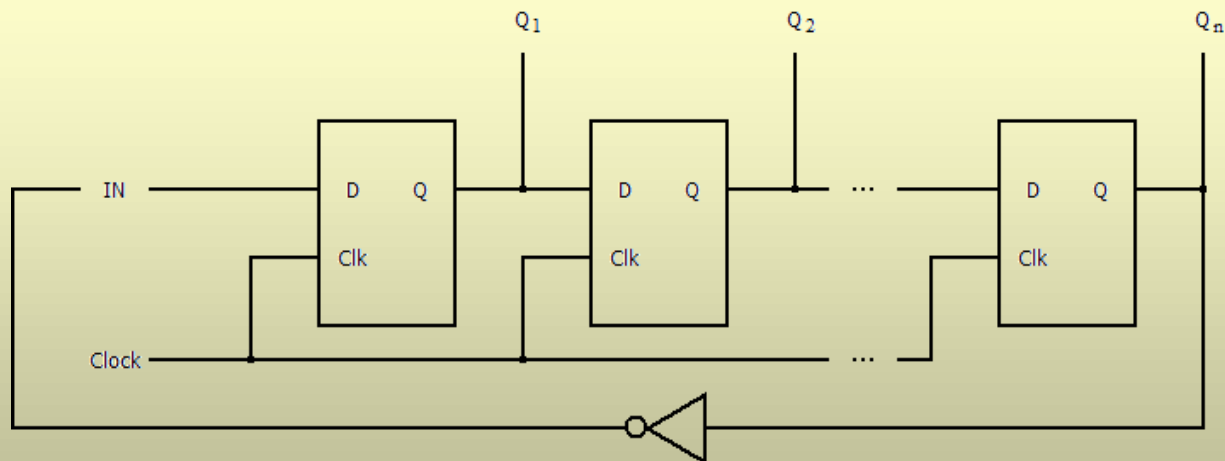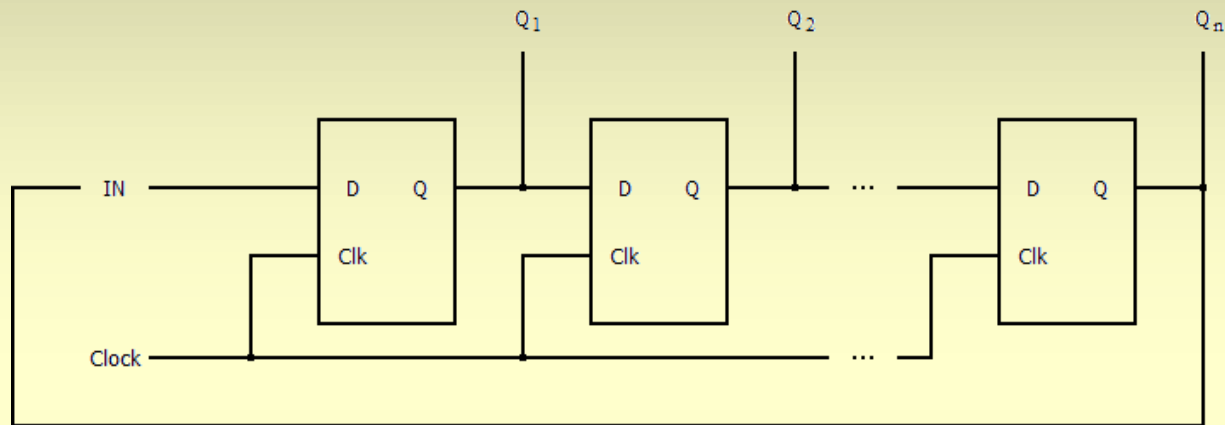

Universal Shift Register

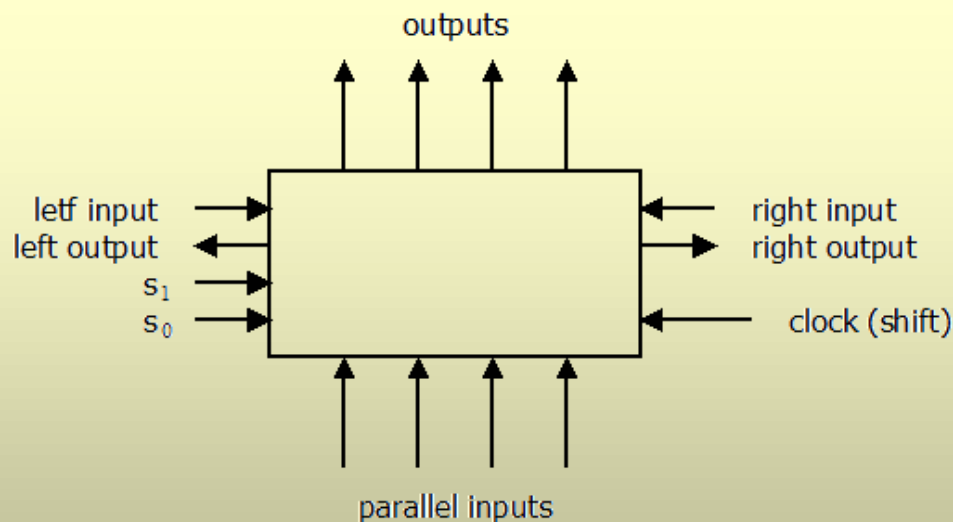- serial or parallel inputs and outputs
- right or left shift operations
- one can use any of the features above, as needed



s_0	s_1	function
0	0	unchanged
0	1	shift right
1	0	shift left
1	1	parallel load

Designing a Sequential Circuit (1)

- finite state machine (automaton)
 1. determine the states of the circuit
 2. determine the state transitions
 - how the next state and the outputs depend on the inputs and the current state
 3. state encoding
 - using the necessary number of bits
 4. write the truth table for the state transitions

Designing a Sequential Circuit (2)

5. minimization

6. implementation

- the state - memorized by flip-flops
- combinational part - from the minimization
 - the inputs of the combinational part (current state) are collected from the outputs of the flip-flops and the input variables
 - the outputs of the combinational part (next state) are applied at the inputs of the flip-flops

Binary Counter

- at each moment keeps an n -bit number
- at each clock "tick" - incrementation
 - could also be decrementation
 - after the maximum value, 0 comes next
 - no inputs, only state variables
 - which keep the current value of the number
 - outputs are identical to the state variables

Example: $n=4$

current state				next state				current state				next state			
q_3	q_2	q_1	q_0	d_3	d_2	d_1	d_0	q_3	q_2	q_1	q_0	d_3	d_2	d_1	d_0
0	0	0	0	0	0	0	1	1	0	0	0	1	0	0	1
0	0	0	1	0	0	1	0	1	0	0	1	1	0	1	0
0	0	1	0	0	0	1	1	1	0	1	0	1	0	1	1
0	0	1	1	0	1	0	0	1	0	1	1	1	1	0	0
0	1	0	0	0	1	0	1	1	1	0	0	1	1	0	1
0	1	0	1	0	1	1	0	1	1	0	1	1	1	1	0
0	1	1	0	0	1	1	1	1	1	1	0	1	1	1	1
0	1	1	1	1	0	0	0	1	1	1	1	0	0	0	0

Example: $n=4$

- by minimization we get the equations below

$$d_0 = \bar{q}_0 = q_0 \oplus 1$$


$$d_1 = \bar{q}_1 \cdot q_0 + q_1 \cdot \bar{q}_0 = q_1 \oplus q_0$$

$$d_2 = \bar{q}_2 \cdot q_1 \cdot q_0 + q_2 \cdot \bar{q}_1 + q_2 \cdot \bar{q}_0 = q_2 \oplus (q_1 \cdot q_0)$$

$$\begin{aligned} d_3 &= \bar{q}_3 \cdot q_2 \cdot q_1 \cdot q_0 + q_3 \cdot \bar{q}_2 + q_3 \cdot \bar{q}_1 + q_3 \cdot \bar{q}_0 = \\ &= q_3 \oplus (q_2 \cdot q_1 \cdot q_0) \end{aligned}$$

– state implementation - D flip-flops

Implementation

 

Microprogramming (1)

- alternative implementation technique
 - the state is still memorized by flip-flops
 - combinational part - implemented by a ROM circuit
 - the inputs of the Boole functions are applied to the address inputs of the ROM
 - the outputs of the Boole functions are collected from the data outputs of the ROM

Microprogramming (2)

- implementation of the combinational part
 - start from the truth table
 - to each location - write the desired output values
- advantage - flexibility
 - any change of the automaton requires only the rewriting of the contents of the ROM
- drawback - low speed
 - ROM circuits are slower than logic gates

The Same Example


- there are 16 ($= 2^4$) states
 - encoded with 4 state bits
- so the ROM circuit will have
 - 2^4 addresses \rightarrow 4 address bits
 - 16 locations
 - 4 data bits \rightarrow locations are 4 bits wide
 - in this example there are no inputs and outputs of the system - only state bits

The Contents of the ROM

address	value
0	0 0 0 1
1	0 0 1 0
2	0 0 1 1
3	0 1 0 0
4	0 1 0 1
5	0 1 1 0
6	0 1 1 1
7	1 0 0 0

address	value
8	1 0 0 1
9	1 0 1 0
10	1 0 1 1
11	1 1 0 0
12	1 1 0 1
13	1 1 1 0
14	1 1 1 1
15	0 0 0 0

Implementation

 

IV. Internal Representations

- elementary internal representations
 - they are part of the computer's architecture
 - so they are implemented in hardware
 - directly accessible to the programmers
- more complex data structures
 - based on elementary representations
 - defined and accessible to the programmers by software

Elementary Representations

- numerical data
 - integer/rational numbers
 - only certain subsets of these sets
- alpha-numerical data
 - characters etc.
- instructions
 - the only system-specific representations
 - thus non-standardized and non-portable

Studying the Representations

- numerical representations
$$\text{repr}(n_1) \text{ op } \text{repr}(n_2) = \text{repr}(n_1 \text{ op } n_2) ???$$
- example - if we add two integer variables, will the result fit into its destination?
- representation errors
 - approximations
 - overflows

Sending the Information

- between various physical media
 - between computers/systems
 - between the components of a computer/system
- transmission errors may occur
 - due to perturbations/incorrect working
 - digital signal - some bits are inverted
 - we wish to detect to occurrence of such errors
 - and even fix them, where possible (correction)

Ways of Detection/Correction

- use additional *redundant* bits
- parity - 1 additional bit
 - allows detecting the occurrence of a (1 bit) error
 - odd/even parity: odd/even number of bits 1
- Hamming code
 - 4 information bits, 3 additional bits
 - detection/correction of multiple errors simultaneously

Example: Odd Parity

- transmitter
 - has to send value $(110)_2$
 - 2 bits of value 1 (even) \rightarrow the additional bit is 1
 - sends $(1101)_2$
- receiver
 - receives the bit string
 - if the number of bits of value 1 is even - error
 - else - eliminate the parity bit and get $(110)_2$

IV.1. Alpha-numerical Codes

Alpha-numerical Codes

- the computer cannot represent characters directly
 - or any non-numerical information: images etc.
- each character is associated a unique number
 - the character is encoded
 - encoding can be at hardware level (elementary representation) or at software level

Standards

- ASCII
 - each character - 7 bits plus one parity bit
- EBCDIC
 - former competitor of ASCII
- ISO 8859-1
 - extends the ASCII code
- Unicode, UCS
 - non-latin characters

ASCII Code

- small letters are assigned consecutive codes
 - in the order given by the English alphabet
 - 'a' - 97; 'b' - 98; ...; 'z' - 122
- similarly - capitals (65, 66, ..., 90)
- similarly - characters that display decimal digits
 - attention: character '0' has code 48 (not 0)
- lexicographic comparison - binary comparison circuit

IV.2. Internal Number Representation

Positional Representation

- also a representation
 - 397 is not a number, but a number representation
- invented by Indians/Arabs
- implicit factor attached to each position in the representation
- essential in computer architecture
 - allows efficient computing algorithms

Base (Radix)

- any natural number $d > 1$
- the set of digits for base d : $\{0, 1, \dots, d-1\}$
- computers work with base $d=2$
 - technically: 2 digits - easiest to implement
 - theoretically: base 2 "matches" Boole logic
 - symbols and operations
 - operations can be implemented by Boole functions

Limits

- in practice, the number of digits is finite
- example - unsigned integers
 - 1 byte wide: $0 \div 2^8 - 1$ (= 255)
 - 2 bytes wide: $0 \div 2^{16} - 1$ (= 65535)
 - 4 bytes wide: $0 \div 2^{32} - 1$ (= 4294967295)
- any number that falls outside the limits cannot be represented correctly

Positional Writing

- consider base $d \in \mathbb{N}^* - \{1\}$
- and the representation given by the string

$$a_{n-1}a_{n-2}\dots a_1a_0a_{-1}\dots a_{-m}$$

- the corresponding number is

$$\sum_{i=-m}^{n-1} (a_i \times d^i) \quad (10)$$

- d^i is the implicit factor for position i
 - including negative powers

Converting from Base d to Base 10

- according to the previous formula
- the decimal point stays in the same position
- example

$$\begin{aligned} 5E4.D_{(16)} &= 5 \times 16^2 + 14 \times 16^1 + 4 \times 16^0 + 13 \\ &\times 16^{-1} = 20480 + 3584 + 64 + 0.8125 = \\ &24128.8125_{(10)} \end{aligned}$$

Converting from Base 10 to Base d

Example: $87.35_{(10)} = 1010111.01(0110)_{(2)}$

integer part

$$87 / 2 = 43 \text{ remainder } 1$$

$$43 / 2 = 21 \text{ remainder } 1$$

$$21 / 2 = 10 \text{ remainder } 1$$

$$10 / 2 = 5 \text{ remainder } 0$$

$$5 / 2 = 2 \text{ remainder } 1$$

$$2 / 2 = 1 \text{ remainder } 0$$

$$1 / 2 = 0 \text{ remainder } 1$$

$$87_{(10)} = 1010111_{(2)}$$

(digits are considered bottom-up)

fractional part

$$0.35 \times 2 = 0.7 + 0$$

$$0.7 \times 2 = 0.4 + 1$$

$$0.4 \times 2 = 0.8 + 0$$

$$0.8 \times 2 = 0.6 + 1$$

$$0.6 \times 2 = 0.2 + 1$$

$$0.2 \times 2 = 0.4 + 0$$

$$0.4 \times 2 = 0.8 + 0$$

(period)

$$0.35_{(10)} = 0.01(0110)_{(2)}$$

Conversions between Bases

- one base is a power of the other base
 - $d_1 = d_2^k \Rightarrow$ to each digit in base d_1 correspond exactly k digits in base d_2
- both bases are powers of the same number n
 - conversion can be made through base n

$$\begin{aligned} 703.102_{(8)} &= 111\ 000\ 011.001\ 000\ 010_{(2)} = \\ &= 0001\ 1100\ 0011.0010\ 0001\ 0000_{(2)} = \\ &= 1C3.21_{(16)} \end{aligned}$$

Approximation and Overflow

- a representation has n digits for the integer part and m digits for the fractional part
 - n and m are finite
- if the number requires more than n digits for the integer part, overflow occurs
- if the number requires more than m digits for the fractional part, approximation occurs
 - at most 2^{-m}

IV.3. BCD and Excess Representations

BCD Representation

- numbers are represented as strings of digits in base 10
 - each digit is represented on 4 bits
- utility
 - business applications (financial etc.)
 - base 10 displays (temperature etc.)
- arithmetical operations - hard to perform
 - addition - cannot simply use a binary adder

BCD Addition (1)

$$\begin{array}{rcl} 5 & = & 0101 + \\ 3 & = & \underline{0011} \\ 8_{(10)} & = & 1000 = 8_{\text{BCD}} \end{array} \qquad \begin{array}{rcl} 5 & = & 0101 + \\ 8 & = & \underline{1000} \\ 13_{(10)} & = & 1101 \\ & \neq & 13_{\text{BCD}} = \\ & = & 0001 \ 0011 \end{array}$$

problems occur when the sum of
the BCD digits exceeds 9

BCD Addition (2)

- solution
 - add 6 (0110) when the sum exceeds 9
- homework: why?

$$5 = \begin{array}{r} 0101 \\ + \end{array}$$

$$8 = \begin{array}{r} 1000 \\ \hline \end{array}$$

$$\begin{array}{r} 1101 \\ + \end{array}$$

$$6 = \begin{array}{r} 0110 \\ \hline \end{array}$$

$$\begin{array}{r} 1\ 0011 \\ \hline \end{array} = 13_{\text{BCD}}$$

$$9 = \begin{array}{r} 1001 \\ + \end{array}$$


$$7 = \begin{array}{r} 0111 \\ \hline \end{array}$$

$$16_{(10)} = \begin{array}{r} 1\ 0000 \\ \hline \end{array} \neq 16_{\text{BCD}}$$

$$6 = \begin{array}{r} 0110 \\ \hline \end{array}$$

$$\begin{array}{r} 1\ 0110 \\ \hline \end{array} = 16_{\text{BCD}}$$

BCD Adder

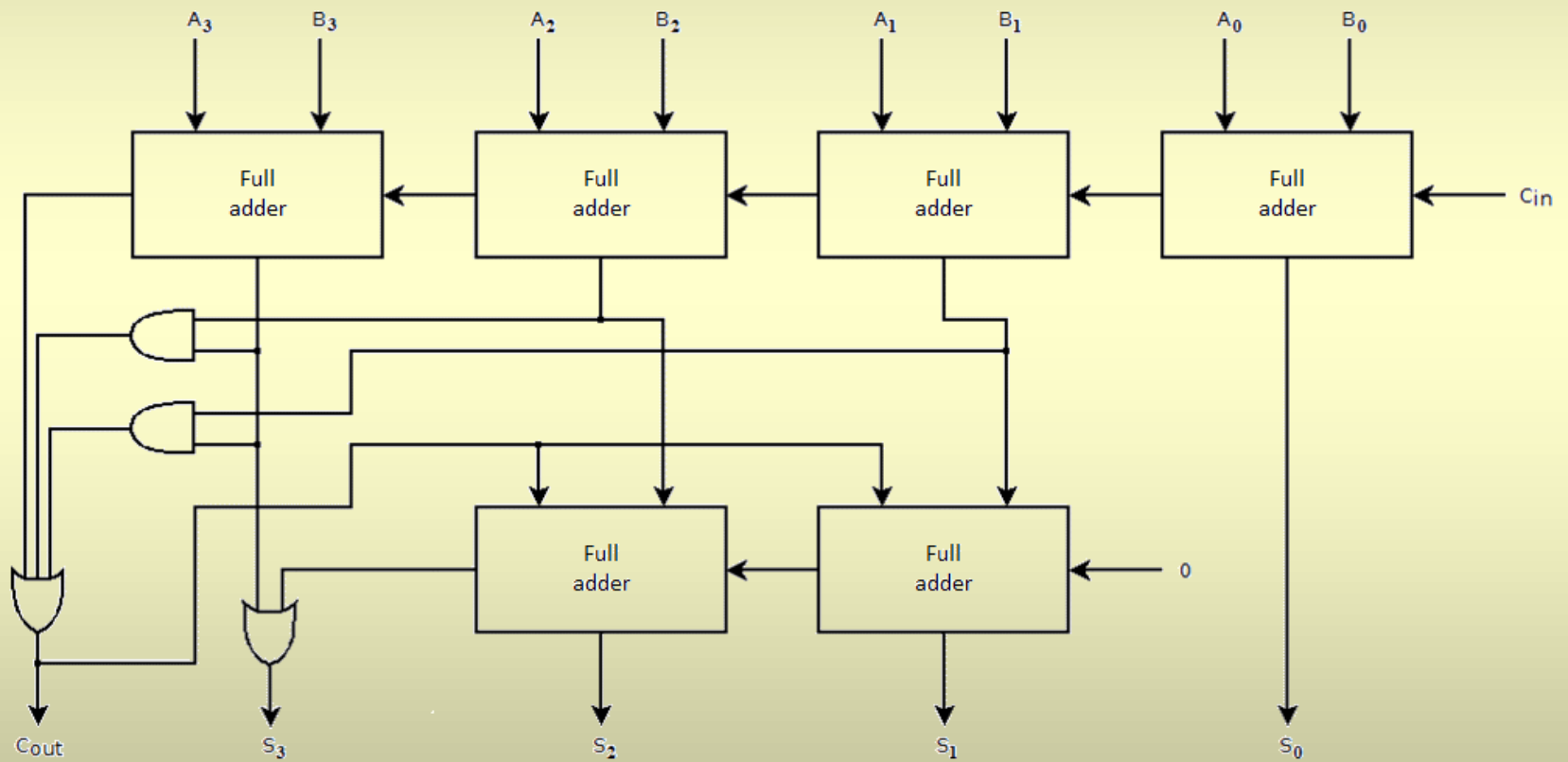

Excess Representation

- based on positional writing
 - non-negative numbers
 - on n bits, the interval of numbers that can be represented is $0 \div 2^n - 1$
- the Excess- k representation
 - for each bit string, subtract k from its value given by positional writing
 - the interval that can be represented: $-k \div 2^n - k - 1$

Example: Excess-5

Binary	Decimal	Excess-5	Binary	Decimal	Excess-5
0000	0	-5	1000	8	3
0001	1	-4	1001	9	4
0010	2	-3	1010	10	5
0011	3	-2	1011	11	6
0100	4	-1	1100	12	7
0101	5	0	1101	13	8
0110	6	1	1110	14	9
0111	7	2	1111	15	10