 


# III. Sequential Circuits

# Sequential Circuit

- at each moment, the output depends on
  - the input
  - the internal state
- so, for the same input, different output values may emerge, at different moments
- internal state
  - memorized by the circuit
  - evolves in time

# Block Diagram



# State Evolution


- the state changes at certain moments
  - synchronous: at regular time moments
    - provided by a special signal (clock)
  - asynchronous: when an event occurs
    - events are defined depending on the circuit's activity
  - why doesn't it change permanently?
    - sending the signals through gates and communication lines - with delays
    - so signals are considered after they have stabilized

# The Clock

- periodic signal
  - active cycle - the percentage of the period when the signal is active
  - depends on what active signal means
    - level-active (during value 0 or 1)
    - edge-active (changing from 0 to 1 or the reverse)
- period duration
  - long enough for the signals to stabilize
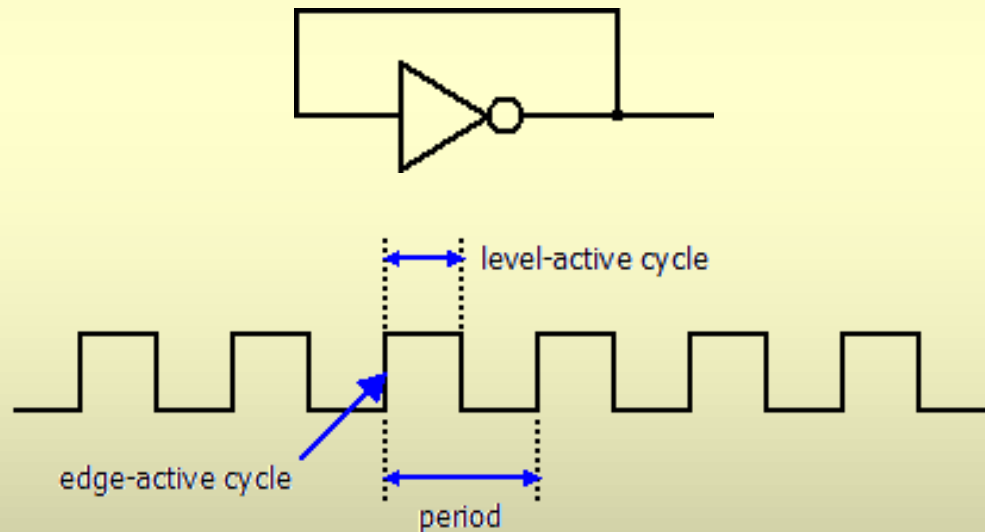
# Implementation

- the simplest logic diagram
  - the feed-back connection is essential



- usually, more complex schemes are used

# Types of Sequential Circuits

- bit-level - bistable circuits
- depending on how the clock is detected
  - *latch* - level-active
  - *flip-flop* - edge-active
- multi-bit circuits
  - registers, counters
  - made of multiple bistable circuits

# III.1. Bistable Circuits




# Bistable Circuit

- what should a bit-implementation circuit look like ?
- specifications
  - can write either 0 or 1 to it
  - memorize the last written value until a new one is written
  - can read the last written value
- cannot be a combinational circuit (memorization)
 
# No-clock RS Bistable Circuit

- two inputs (R,S), two outputs (Q,P), two feed-back connections
  - the circuit implements a single bit:  $P = \bar{Q}$



## How It Works (1)

- at first sight we have simultaneously
$$q = Q \text{ and } p = P$$
$$Q = \overline{p + R}$$
$$P = \overline{q + S}$$
- in fact, when inputs change, outputs do not change instantly
  - due to gate propagation delays
  - so the behavior can be studied with truth tables

## How It Works (2)

- consider (q,p) the current output values
- and (Q,P) the next output values
  - depending on (q,p) and on inputs (R,S)
  - they will become current values after the propagation delays

Karnaugh Diagram

outputs: QP

qp\RS	00	01	11	10
00	11	10	00	01
01	01	00	00	01
11	00	00	00	00
10	10	10	00	00

$$Q = \overline{p} + R$$

$$P = q + \overline{S}$$

# Stable States

- in principle,  $(Q,P)$  changes permanently
- but when  $(Q,P)=(q,p)$ , we have a stable state
  - we want to find these stable states
  - the circuit can be controlled if passing only through stable states

qp\RS	00	01	11	10
00	11	10	<b>00</b>	01
01	<b>01</b>	00	00	<b>01</b>
11	00	00	00	00
10	<b>10</b>	<b>10</b>	00	00

# Functioning (1)

initial state (q,p)	evolution (q,p)	conclusion
$R=0, S=1$		
00	00 $\rightarrow$ 10 stable	the circuit evolves towards the stable state (Q,P)=(1,0) in all cases
01	01 $\rightarrow$ 00 $\rightarrow$ 10 stable	
10	10 stable	
11	11 $\rightarrow$ 00 $\rightarrow$ 10 stable	
$R=1, S=0$		
00	00 $\rightarrow$ 01 stable	the circuit evolves towards the stable state (Q,P)=(0,1) in all cases
01	01 stable	
10	10 $\rightarrow$ 00 $\rightarrow$ 01 stable	
11	11 $\rightarrow$ 00 $\rightarrow$ 01 stable	

# Functioning (2)

initial state (q,p)	evolution (q,p)	conclusion
$R=0, S=0$		
00	$00 \rightarrow 11 \rightarrow 00 \rightarrow \dots$	for $q=p$ , the circuit oscillates indefinitely  for $q \neq p$ , the circuit holds the state (stable)
01	01 stable	
10	10 stable	
11	$11 \rightarrow 00 \rightarrow 11 \rightarrow \dots$	
$R=1, S=1$		
00	00 stable	the circuit evolves towards the stable state (Q,P)=(0,0) in all cases
01	$01 \rightarrow 00$ stable	
10	$10 \rightarrow 00$ stable	
11	$11 \rightarrow 00$ stable	

## Functioning (3)


- we remind the condition  $P = \bar{Q}$
- $(R,S)=(0,0)$ : keep the current state  
(memorization)
- $(R,S)=(0,1)$ : stabilize at  $Q=1$  (set)
- $(R,S)=(1,0)$ : stabilize at  $Q=0$  (reset)
- $(R,S)=(1,1)$ : forbidden combination
- because  $P=Q$  - does not implement a bit



# Synchronous Sequential Circuits

- add a synchronization signal (clock) to the RS bistable circuit
- starting from which other bistable circuits can be designed
  - D, JK, T
- all are latches (level-active)


# RS Latch

 

$q(=Q_t)$	R	S	$Q_{t+1}$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	*
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	*

 
# D Latch

- models only  $R \neq S$  situations
- eliminates the forbidden combination
- with this circuit, the current state does not actually depend on the previous one


 
# JK Latch


- eliminates the RS forbidden combination



$q(=Q_t)$	J	K	$Q_{t+1}$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0
 
# T Latch

- derived from the JK latch
- models only J=K situations



$q(=Q_t)$	T	$Q_{t+1}$
0	0	0
0	1	1
1	0	1
1	1	0

# State Evolution





R	S	$Q_{t+1}$	
0	0	$Q_t$	unchanged
0	1	1	write 1
1	0	0	write 0
1	1	*	forbidden

J	K	$Q_{t+1}$	
0	0	$Q_t$	unchanged
0	1	0	write 0
1	0	1	write 1
1	1	$\overline{Q_t}$	invert

D	$Q_{t+1}$	
0	0	write 0
1	1	write 1

T	$Q_{t+1}$	
0	$Q_t$	unchanged
1	$\overline{Q_t}$	invert

# Block Diagrams for Latches

    

# Homework


- implement and analyze the behavior of the no-clock RS circuit using NAND gates instead of the NOR gates
- the same for the RS, D, JK, T latches



# Flip-flop

- inputs are considered on the rising (or falling) edge of the clock signal
- ways of making a flip-flop
  - electronics - derive the clock signal
    - results in an impulse-like signal
  - use latches → master-slave circuits

# Master-slave D Flip-flop

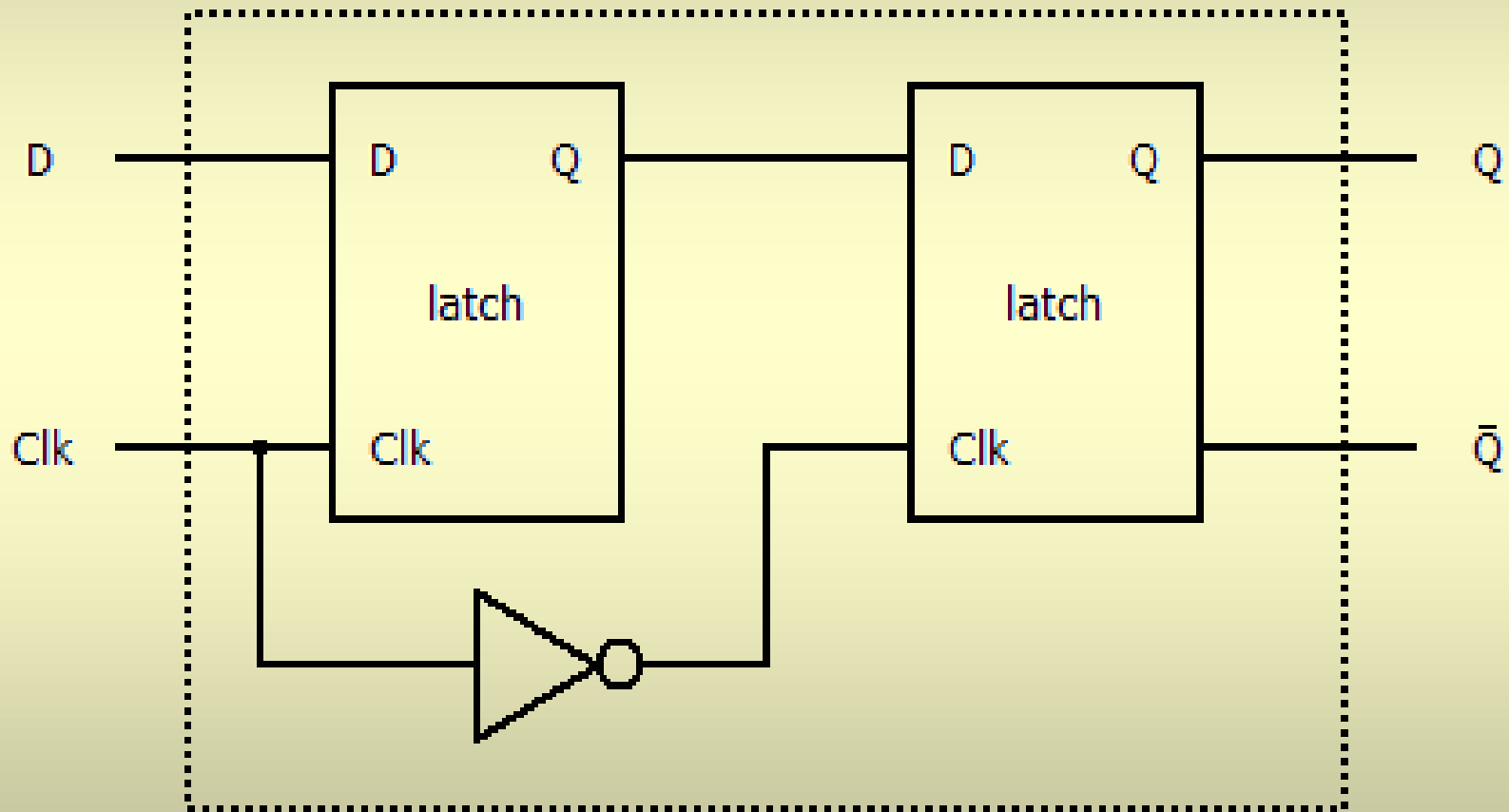

# Latch vs. Flip-flop

- each category has its utility
- flip-flops - used for controlling digital systems
  - the edge of the clock signal is very short compared with the clock period
    - i.e., it can be considered as a moment
  - during each clock period, the system makes exactly one step of its evolution
- latches - asynchronous systems


## III.2. Complex Sequential Circuits

# Registers

- a bistable circuit implements a single bit
  - not very useful in practice
- we can use several bistable circuits together
  - all receive the same command at the same time
  - such a circuit is called register
- types of registers
  - parallel registers
  - shift (serial) registers

 
# Parallel Register

- implementation with D bistable circuits
  - can be latches or flip-flops, as needed
- the same command (clock)
  - all bits change at the same moments
- natural extension of the bistable circuit




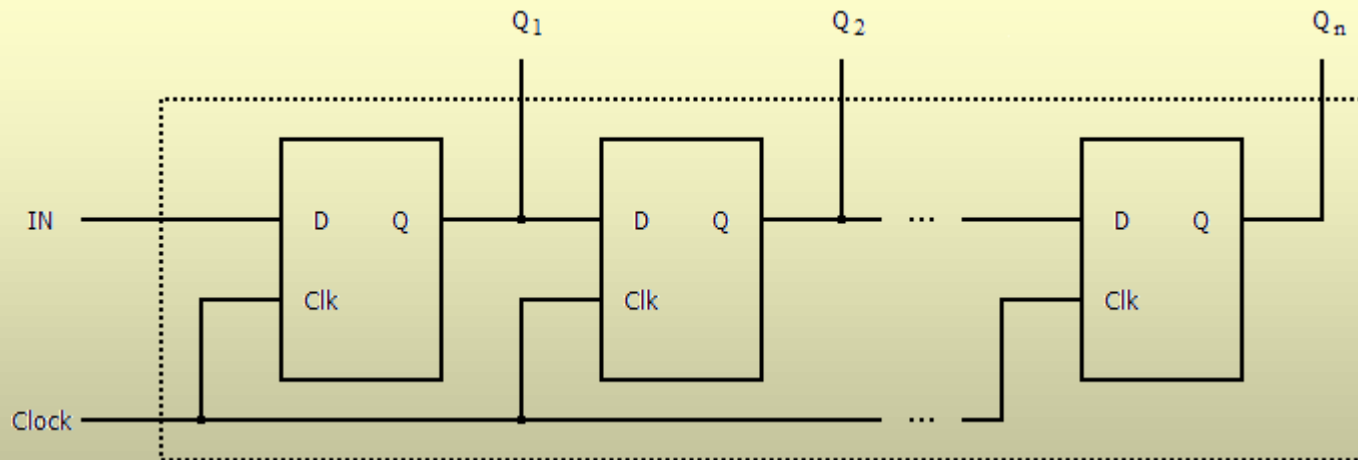
# Classic Shift Register

- memorizes the last  $n$  values applied on the input
- can be implemented only with flip-flops
  - homework: why?




# Other Shift Registers

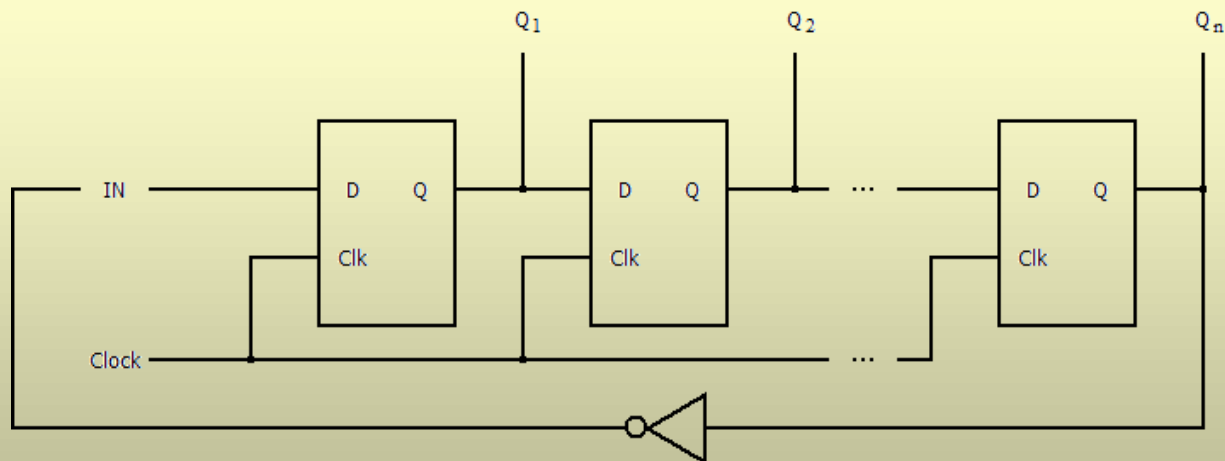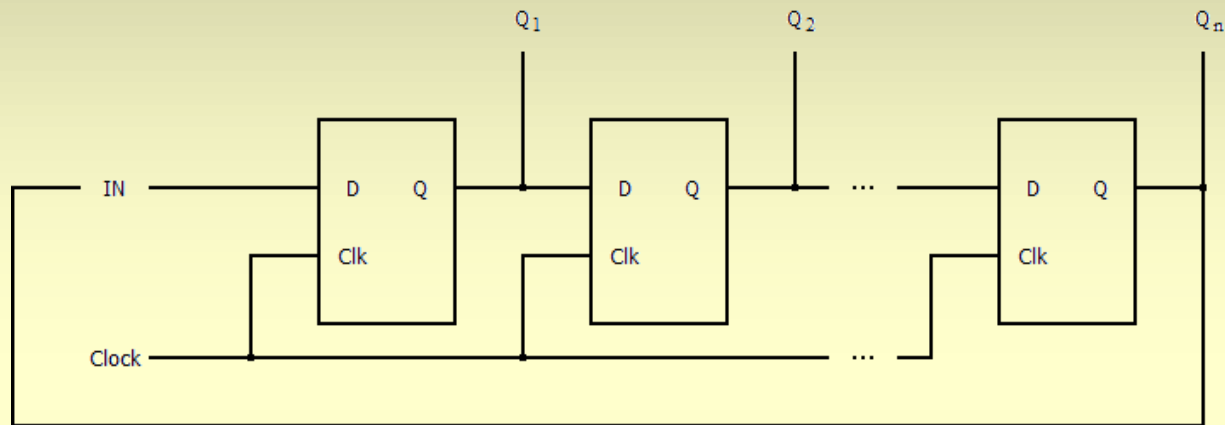


 
# Universal Shift Register

- serial or parallel inputs and outputs
- right or left shift operations
- one can use any of the features above, as needed



$s_0$	$s_1$	function
0	0	unchanged
0	1	shift right
1	0	shift left
1	1	parallel load

# Designing a Sequential Circuit (1)

- finite state machine (automaton)
  1. determine the states of the circuit
  2. determine the state transitions
    - how the next state and the outputs depend on the inputs and the current state
  3. state encoding
    - using the necessary number of bits
  4. write the truth table for the state transitions

# Designing a Sequential Circuit (2)

5. minimization

6. implementation

- the state - memorized by flip-flops
- combinational part - from the minimization
  - the inputs of the combinational part (current state) are collected from the outputs of the flip-flops and the input variables
  - the outputs of the combinational part (next state) are applied at the inputs of the flip-flops

# Binary Counter

- at each moment keeps an  $n$ -bit number
- at each clock "tick" - incrementation
  - could also be decrementation
  - after the maximum value, 0 comes next
  - no inputs, only state variables
    - which keep the current value of the number
  - outputs are identical to the state variables

# Example: $n=4$

current state				next state				current state				next state			
$q_3$	$q_2$	$q_1$	$q_0$	$d_3$	$d_2$	$d_1$	$d_0$	$q_3$	$q_2$	$q_1$	$q_0$	$d_3$	$d_2$	$d_1$	$d_0$
0	0	0	0	0	0	0	1	1	0	0	0	1	0	0	1
0	0	0	1	0	0	1	0	1	0	0	1	1	0	1	0
0	0	1	0	0	0	1	1	1	0	1	0	1	0	1	1
0	0	1	1	0	1	0	0	1	0	1	1	1	1	0	0
0	1	0	0	0	1	0	1	1	1	0	0	1	1	0	1
0	1	0	1	0	1	1	0	1	1	0	1	1	1	1	0
0	1	1	0	0	1	1	1	1	1	1	0	1	1	1	1
0	1	1	1	1	0	0	0	1	1	1	1	0	0	0	0

## Example: $n=4$

- by minimization we get the equations below

$$d_0 = \overline{q_0} = q_0 \oplus 1$$


$$d_1 = \overline{q_1} \cdot q_0 + q_1 \cdot \overline{q_0} = q_1 \oplus q_0$$

$$d_2 = \overline{q_2} \cdot q_1 \cdot q_0 + q_2 \cdot \overline{q_1} + q_2 \cdot \overline{q_0} = q_2 \oplus (q_1 \cdot q_0)$$

$$\begin{aligned} d_3 &= \overline{q_3} \cdot q_2 \cdot q_1 \cdot q_0 + q_3 \cdot \overline{q_2} + q_3 \cdot \overline{q_1} + q_3 \cdot \overline{q_0} = \\ &= q_3 \oplus (q_2 \cdot q_1 \cdot q_0) \end{aligned}$$

– state implementation - D flip-flops

# Implementation

 

# Microprogramming (1)

- alternative implementation technique
  - the state is still memorized by flip-flops
  - combinational part - implemented by a ROM circuit
  - the inputs of the Boole functions are applied to the address inputs of the ROM
  - the outputs of the Boole functions are collected from the data outputs of the ROM



## Microprogramming (2)

- implementation of the combinational part
  - start from the truth table
  - to each location - write the desired output values
- advantage - flexibility
  - any change of the automaton requires only the rewriting of the contents of the ROM
- drawback - low speed
  - ROM circuits are slower than logic gates

# The Same Example


- there are 16 ( $= 2^4$ ) states
  - encoded with 4 state bits
- so the ROM circuit will have
  - $2^4$  addresses  $\rightarrow$  4 address bits
    - 16 locations
  - 4 data bits  $\rightarrow$  locations are 4 bits wide
  - in this example there are no inputs and outputs of the system - only state bits

# The Contents of the ROM

address	value
0	0 0 0 1
1	0 0 1 0
2	0 0 1 1
3	0 1 0 0
4	0 1 0 1
5	0 1 1 0
6	0 1 1 1
7	1 0 0 0

address	value
8	1 0 0 1
9	1 0 1 0
10	1 0 1 1
11	1 1 0 0
12	1 1 0 1
13	1 1 1 0
14	1 1 1 1
15	0 0 0 0

# Implementation

 

# IV. Internal Representations

- elementary internal representations
  - they are part of the computer's architecture
  - so they are implemented in hardware
  - directly accessible to the programmers
- more complex data structures
  - based on elementary representations
  - defined and accessible to the programmers by software

# Elementary Representations

- numerical data
  - integer/rational numbers
  - only certain subsets of these sets
- alpha-numerical data
  - characters etc.
- instructions
  - the only system-specific representations
  - thus non-standardized and non-portable

# Studying the Representations

- numerical representations
$$\text{repr}(n_1) \text{ op } \text{repr}(n_2) = \text{repr}(n_1 \text{ op } n_2) ???$$
- example - if we add two integer variables, will the result fit into its destination?
- representation errors
  - approximations
  - overflows



# Sending the Information

- between various physical media
  - between computers/systems
  - between the components of a computer/system
- transmission errors may occur
  - due to perturbations/incorrect working
  - digital signal - some bits are inverted
  - we wish to detect to occurrence of such errors
  - and even fix them, where possible (correction)

# Ways of Detection/Correction

- use additional *redundant* bits
- parity - 1 additional bit
  - allows detecting the occurrence of a (1 bit) error
  - odd/even parity: odd/even number of bits 1
- Hamming code
  - 4 information bits, 3 additional bits
  - detection/correction of multiple errors simultaneously

## Example: Odd Parity

- transmitter
  - has to send value  $(110)_2$
  - 2 bits of value 1 (even)  $\rightarrow$  the additional bit is 1
  - sends  $(1101)_2$
- receiver
  - receives the bit string
  - if the number of bits of value 1 is even - error
  - else - eliminate the parity bit and get  $(110)_2$